

Kapasitansi / kapasitor

$$Z_c = \frac{1}{\omega C} \lll$$

Elektrikal kapasitor

Interfacial kapasitor $Z_c = \infty$

$f \lll$

PF

\rightarrow f rendah
di open

$$\omega = 2\pi f$$

$f \ggg$

$$Z_c = \frac{1}{\omega C} = \lll$$

$Z_c \ggg \rightarrow$ sangat besar
 ∞

Intensitas kapasitansi → Jika frekuensi rendah dan nilai C kecil
(PF) → $Z = \frac{1}{\omega C} = \infty$ → open circuit

Sehingga efek kapasitansi di BJT diabaikan

Jika frekuensi rendah

$$Z_C = \frac{1}{\omega C} = \frac{1}{\omega \gg C \ll} \rightarrow \text{??? ada masalah}$$

tinggi → ∞ → turun

Saat f tinggi with kapasitansi internal maka Z turun
maka mempengaruhi nilai dari penguatan.

Kapasitor Elektrolysis \rightarrow nilai kapasitansi besar (NF)

$$Z_c = \frac{1}{\omega C} = \frac{1}{\omega C \gg}$$

$$\omega C \gg$$

$Z_c \ll \rightarrow$ cenderung Short circuit

$$\omega = 2\pi f$$

$$f \ll$$

$$f \gg$$


$$Z_c = \frac{1}{\omega C} = \frac{1}{\omega \gg C \gg} = \text{SC}$$

$$Z_c = \frac{1}{\omega C} = \frac{1}{\omega \ll C} \rightarrow Z_c \rightarrow \text{ada}$$

kecil \rightarrow menbisa
berpengaruh pd rangkaian


Kesimpulan

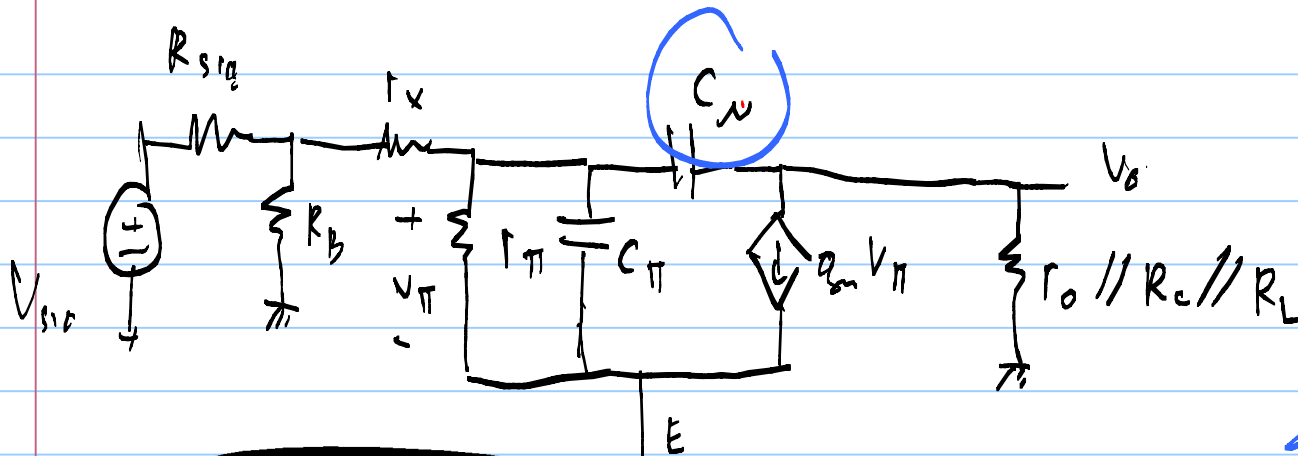1. Frekuensi tinggi yg berpengaruh ke kapasitansi internal sedang ke kapasitansi elektron short circuit
2. Frekuensi rendah yg berpengaruh ke kapasitansi elektron sedang ke kapasitansi internal open circuit



$$Z_1 = Z$$

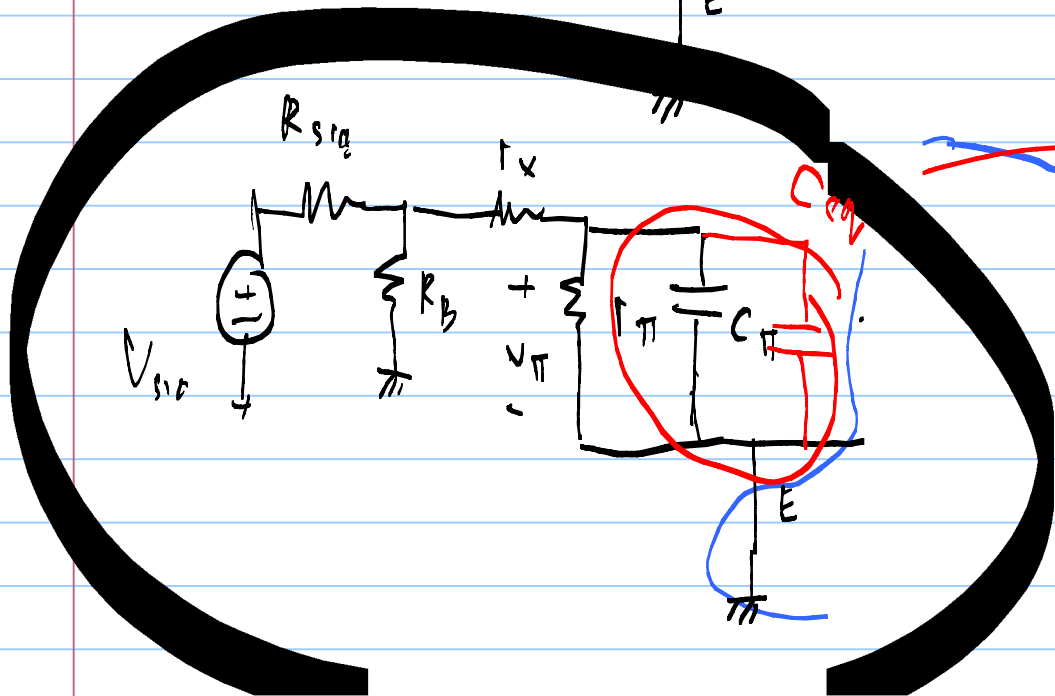
$$\frac{1}{\omega C_{eq}} = \frac{1}{\omega C_{\mu} (1 - A_v)}$$



$$C_{\pi} + C_{eq}$$

$$V_o = -f_o // R_c // R_L$$

$$C_{eq} = C_{\mu} (1 - A_v)$$

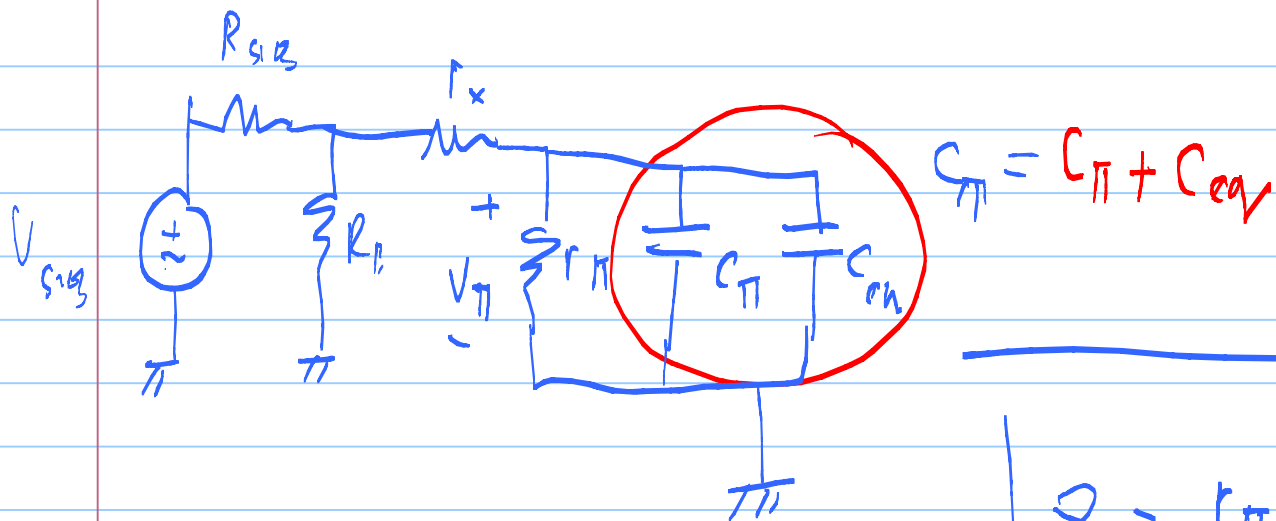

$$Z = r_{\pi} \parallel X_{C_{\pi}} = \frac{r_{\pi} \cdot \frac{1}{sC_{\pi}}}{r_{\pi} + \frac{1}{sC_{\pi}}}$$

