
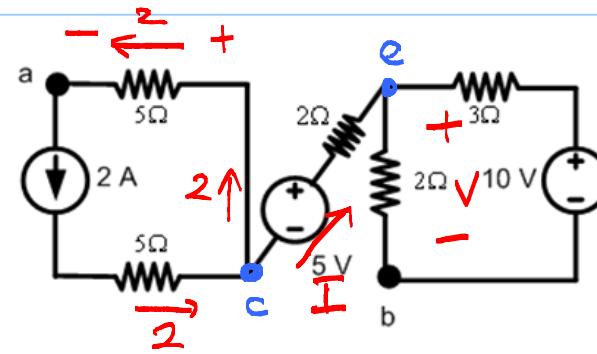




1

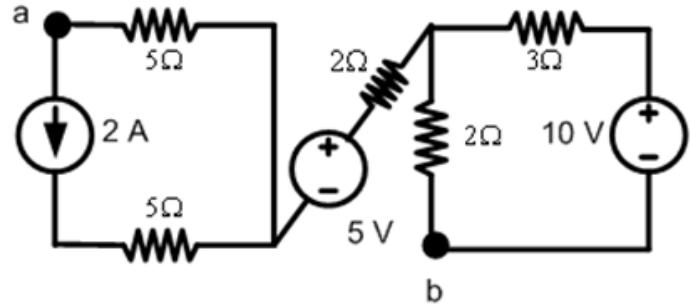

$$\begin{aligned}\sum I &= 0 \\ I + 2 &= 2 \\ I &= 0 \\ V &= \frac{2}{2+3} \times 10 = 4\end{aligned}$$

$$\begin{aligned}V_{ab} &= V_{ac} + V_{ce} + V_{eb} \\ &= (-2 \times 5) - 5 + (2 \times I) + V \\ &= -10 - 5 + 2.0 + 4 \\ &= \boxed{-11 \text{ V}}\end{aligned}$$

(2)

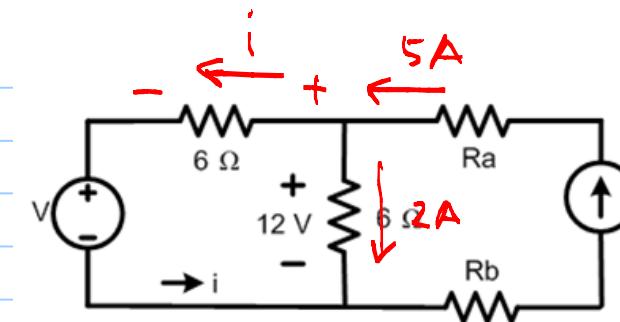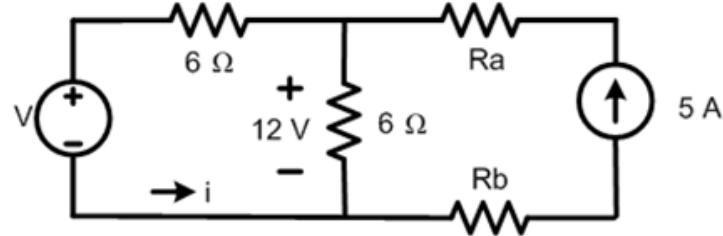

$$\begin{aligned}\Sigma I &= 0 \\ 5 &= i + 2 \\ i &= 3\text{ A}\end{aligned}$$


$$\Sigma V = 0$$

$$-V - (i \times 6) + 12 = 0$$


$$V = 12 - (i \times 6)$$

$$V = 12 - (3 \times 6) = 12 - 18 = -6\text{ V}$$

(3)

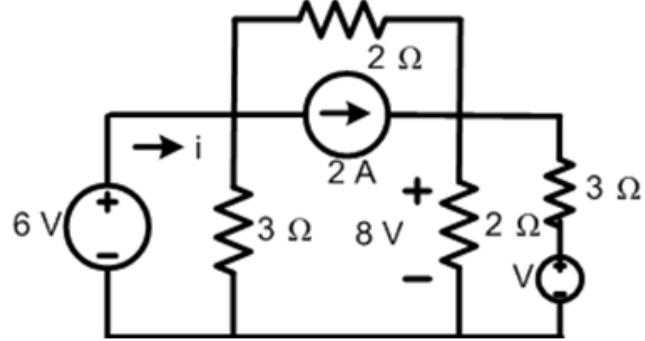

⇒

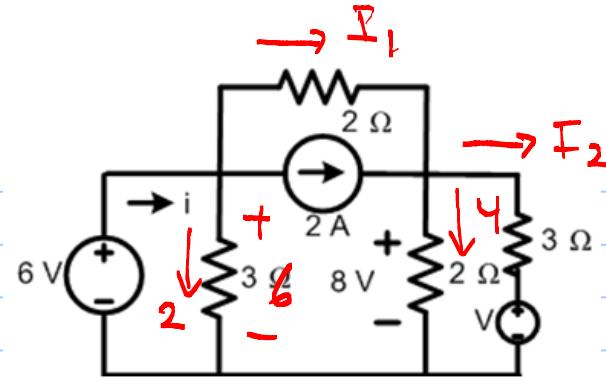

$$\sum V = 0$$

$$-6 + 2I_1 + 8 = 0$$

$$I_1 = \frac{2}{-2} = -1$$

$$i - 4 = -1$$

$$i = 3 \text{ A}$$

$$\sum V = 0$$

$$3I_2 + V - 8 = 0$$



$$V = 8 - 3I_2 = 8 - 3(i - 6) = 8 - 3(3 - 6)$$

$$V = 8 + 9 = 17 \text{ V}$$

$$\begin{aligned}\sum I &= 0 \\ i &= 2 + 2 + I_1 \\ I_1 &= (i - 4)\end{aligned}$$

$$\begin{aligned}\sum I &= 0 \\ I_1 + 2 &= I_2 + 4 \\ I_2 &= I_1 + 2 - 4 \\ I_2 &= (i - 4) - 2 \\ I_2 &= (i - 6)\end{aligned}$$



4

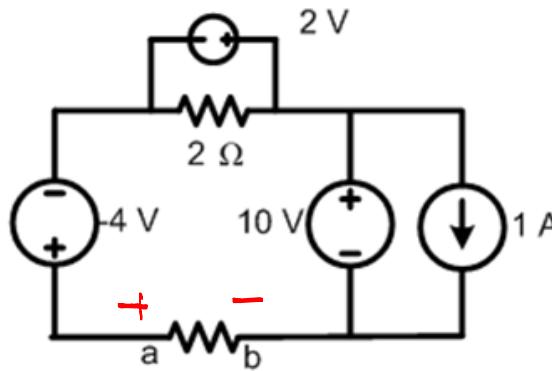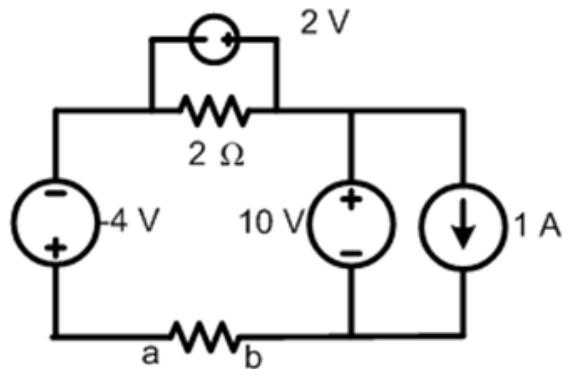

$$\sum V = 0$$

$$V_{ab} - 10 + 2 - (-4) = 0$$

$$V_{ab} = 10 - 2 - 4 = \text{uV}$$

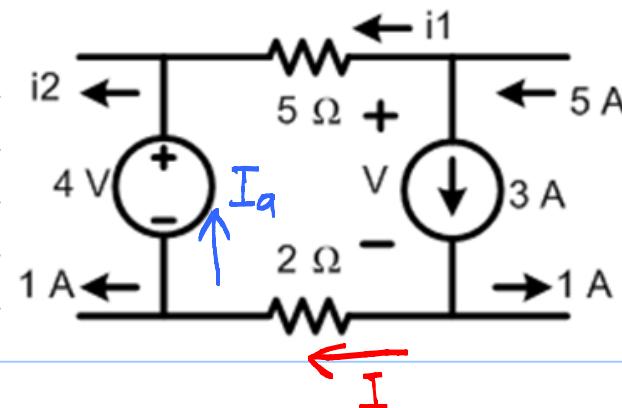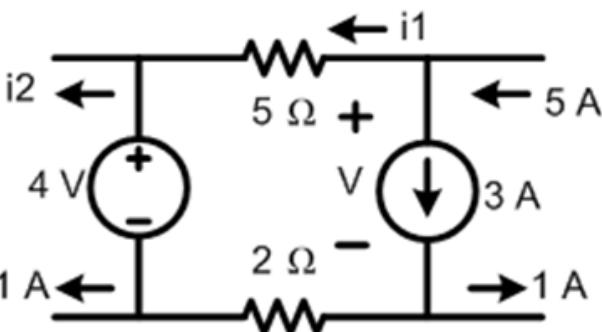

$$\sum I = 0$$

$$3 = I + I$$

$$I = 2A$$

$$\sum I = 0$$

$$I = I_q + I$$

$$I_q = 2 - 1 = 1A$$

$$\sum I = 0$$



$$5 = i_1 + 3$$

$$i_1 = 5 - 3 = 2A$$

$$\sum I = 0$$

$$i_2 = i_1 + I_q = 2 + 1$$

$$i_2 = 3A$$

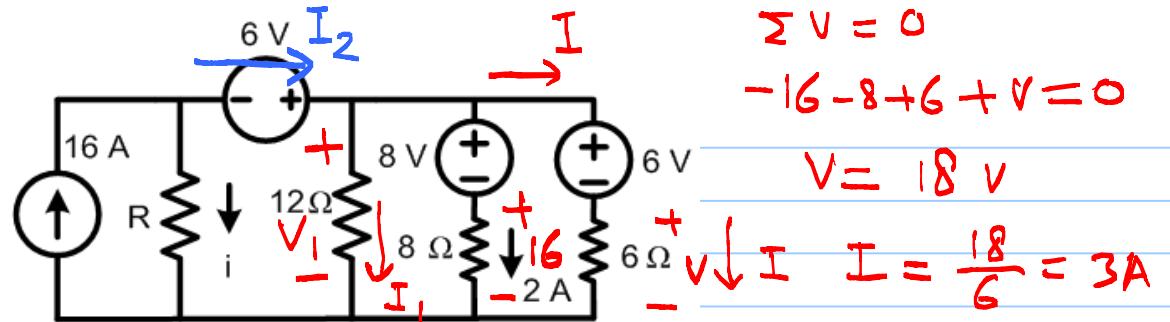
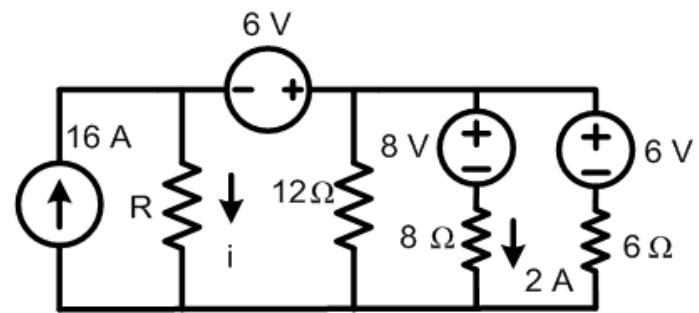


$$\begin{aligned}\sum V &= 0 \\ -V_1 + 8 + 16 &= 0 \\ V_1 &= 24 \text{ V}\end{aligned}$$

$$\begin{aligned}\sum I &= 0 \\ I_2 &= I_1 + 2 + I = 3 + 2 + 3 = 8 \text{ A}\end{aligned}$$

$$\begin{aligned}I_1 &= \frac{24}{8} = 3 \text{ A} \\ i &= 16 - I_2 = 16 - 8 = 8 \text{ A}\end{aligned}$$
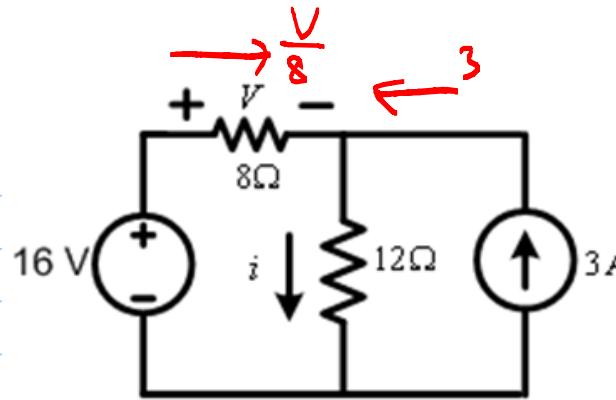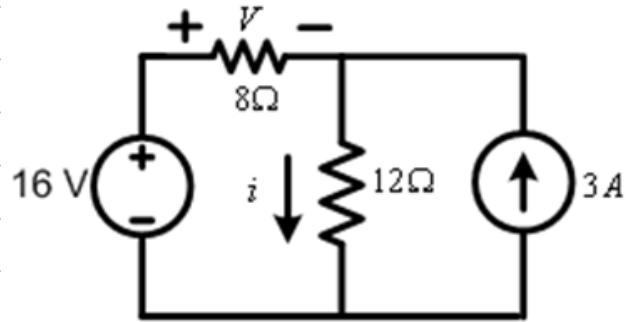
$$\begin{aligned}\sum V &= 0 \\ -6 + V_1 - iR &= 0 \\ R &= \frac{V_1 - 6}{i} = \frac{24 - 6}{8} = \frac{18}{8} = \frac{9}{4} \Omega\end{aligned}$$



$$i = \frac{V}{8} + 3$$

$$i = -\frac{8}{8} + 3 \quad \textcircled{=} 2A$$

$$\sum I = 0$$

$$i = \frac{V}{8} + 3$$

$$\sum V = 0$$

$$-16 + V + 12i = 0$$

$$-16 + V + 12 \left(\frac{V}{8} + 3 \right) = 0$$



$$-16 + V + \frac{12V}{8} + 36 = 0$$

$$-128 + 8V + 12V + 288 = 0$$

$$20V + 160 = 0$$

$$V = -\frac{160}{20} = \textcircled{-8V}$$

(8)

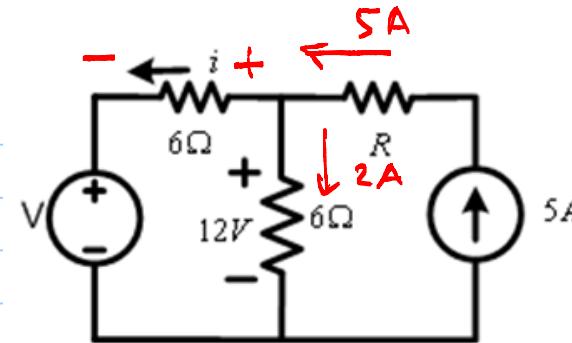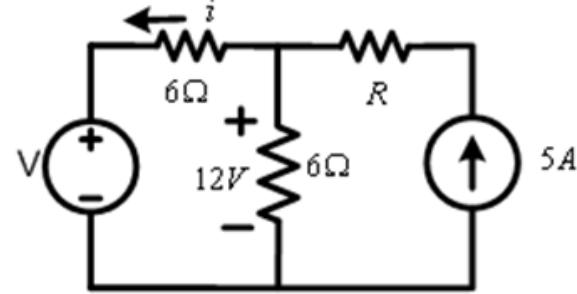

$$\sum i = 0$$

$$5 = i + 2$$

$$i = 5 - 2 = 3A$$



$$\sum V = 0$$

$$-V - 6i + 12 = 0$$

$$V = 12 - 6i$$

$$V = 12 - (6 \times 3) = 12 - 18$$

$$V = \boxed{-6V}$$

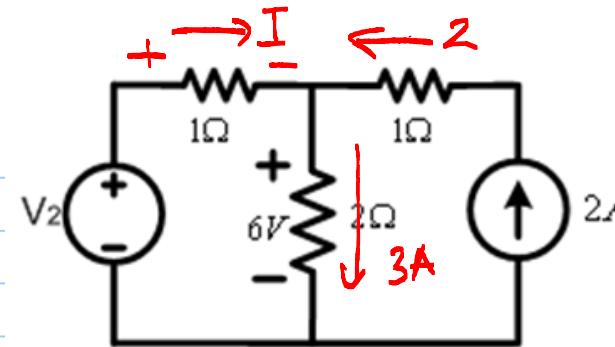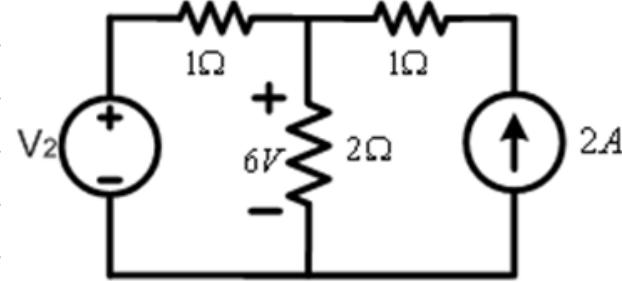

$$\sum I = 0$$

$$I + 2 = 3$$



$$I = 3 - 2 = 1A$$

$$\sum V = 0$$



$$-V_2 + I \cdot 1\Omega + 6V = 0$$

$$V_2 = 6 + 1 \cdot I = 6 + 1$$

$V_2 = 7V$

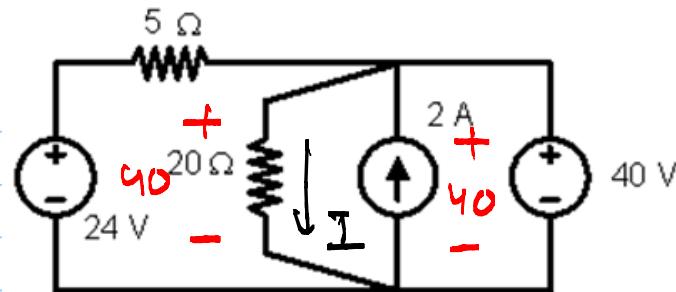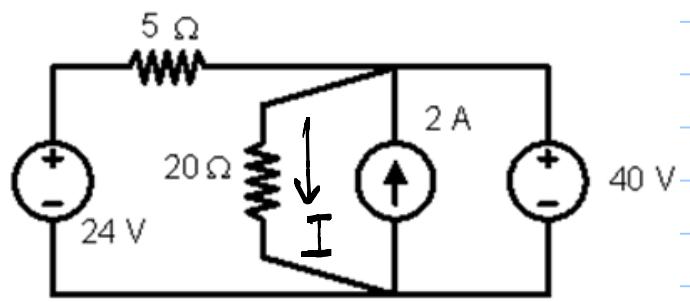

$$I = \frac{40}{20} = 2\text{ A}$$

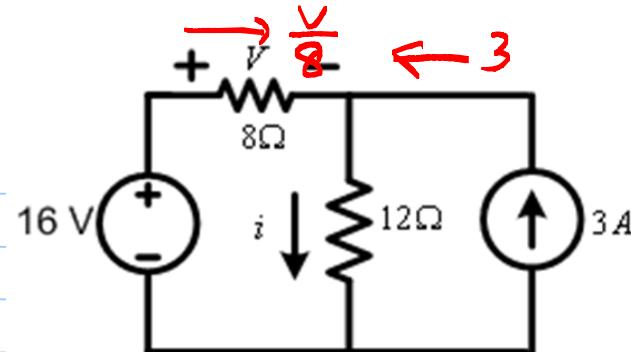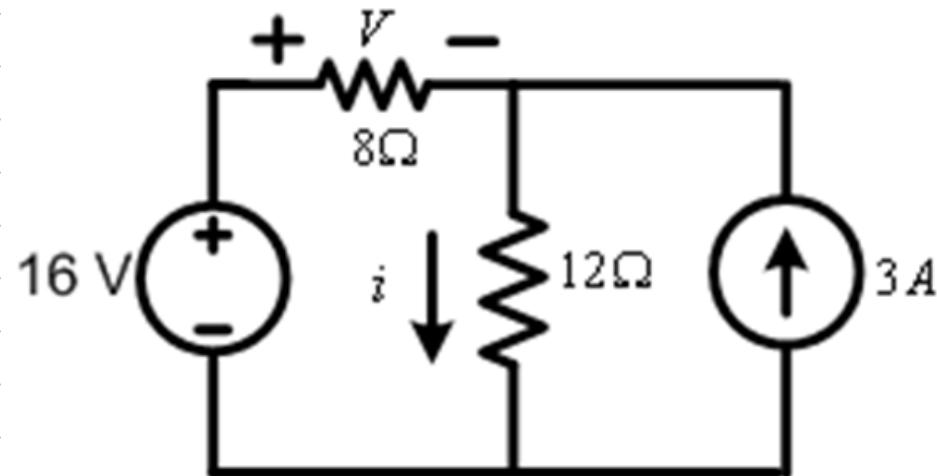

$$\sum I = 0$$

$$i = \frac{V}{8} + 3$$

$$\sum V = 0$$

$$-16 + V + 12i = 0$$

$$-16 + V + 12\left(\frac{V}{8} + 3\right) = 0$$



$$-16 + V + \frac{12V}{8} + 36 = 0$$

$$-128 + 8V + 12V + 288 = 0$$



$$20V + 160 = 0$$

$$V = -8 \text{ V}$$

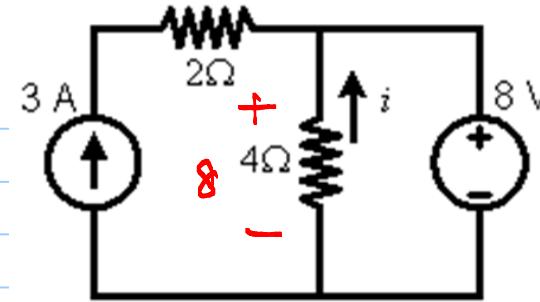
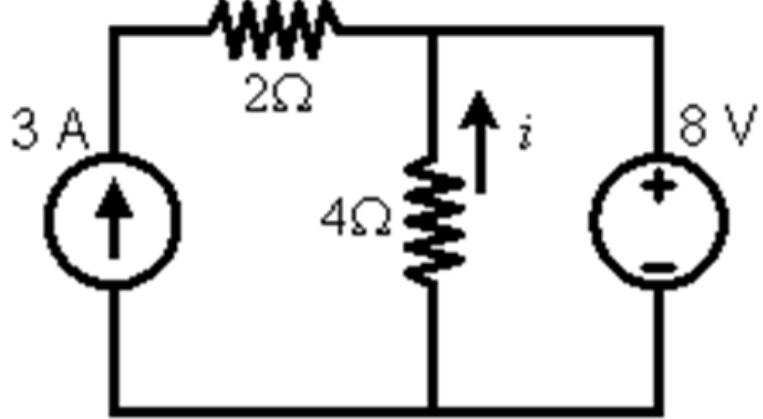
$$i = \frac{V}{3} + 3 = -\frac{8}{3} + 3 = 2 \text{ A}$$



$$i = \frac{8}{4} = 2A$$

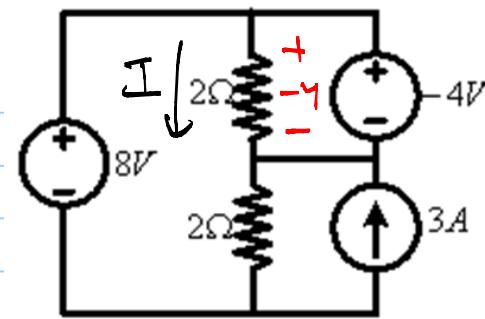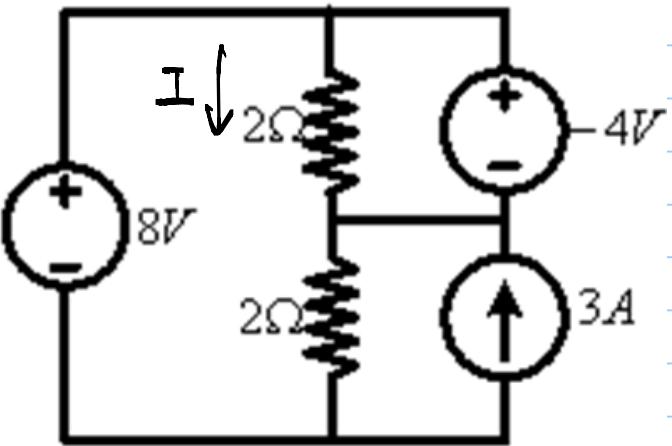

$$I = -\frac{4}{2} = -2A$$

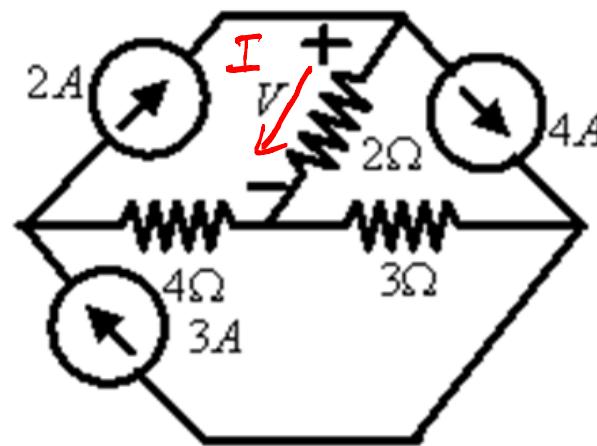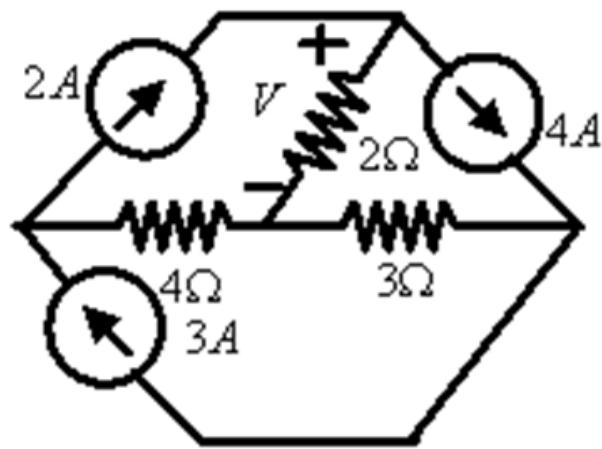

$$\sum I = 0$$

$$2 = I + 4$$

$$I = -2A$$

$$V = 2I = 2 \times (-2)$$

$$V = -4V$$

