

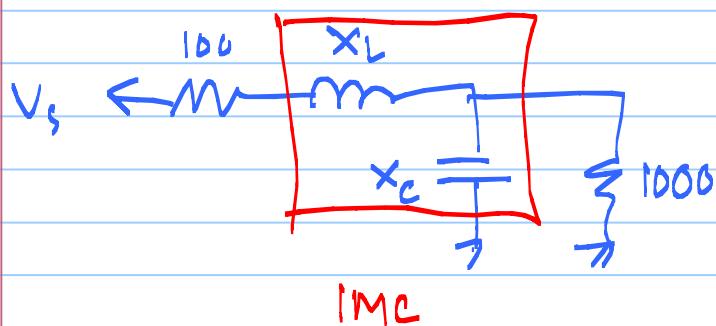


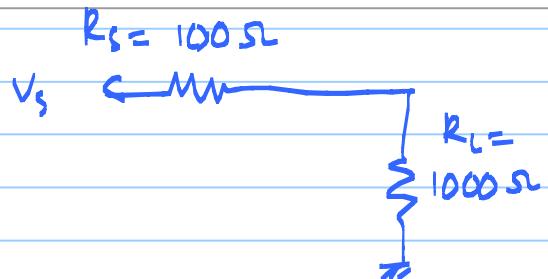Rancang suatu IMC bentuk "L" yang menyepadankan $R_s = 100\Omega$ dan $R_L = 1K\Omega$ pada $f = 100MHz$, dengan sifat meloloskan sinyal DC.



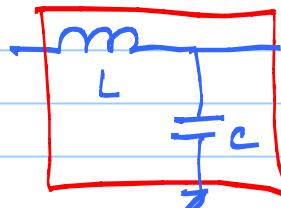Karena $R_s < R_L$ maka IMC L Kanan dan meloloskan DC \rightarrow LPF



IMC L Kanan

$$Q_p = Q_s = \sqrt{\frac{R_p}{R_s}} - 1 = \sqrt{\frac{1000}{100}} - 1 = 3$$



$$Q_s = \frac{X_s}{R_s} = \frac{X_L}{100} \rightarrow X_L = 3 \times 100 = 300 \text{ } \Omega$$

$$2\pi f_r L = 300$$

$$L = \frac{300}{2\pi \cdot 100 \cdot 10^9} = 477 \text{ nH}$$

$$Q_p = \frac{R_p}{X_p} = \frac{1000}{X_C} \rightarrow X_C = \frac{1000}{3} = 333$$
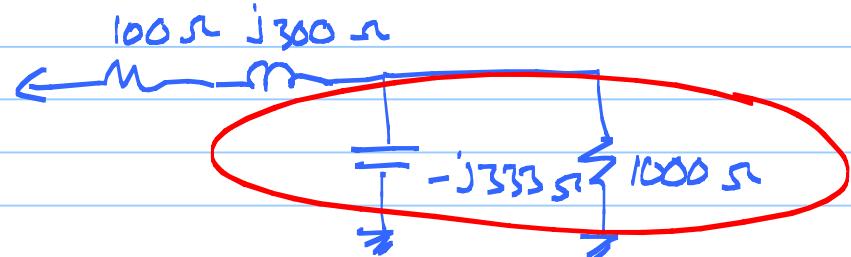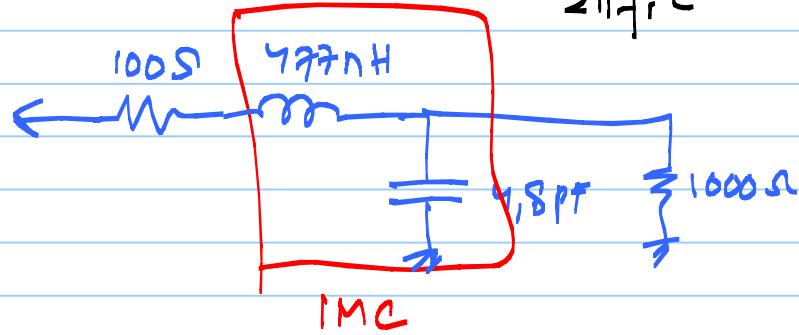
$$\frac{1}{2\pi f_c C} = 333 \rightarrow C = \frac{1}{2\pi \cdot 100 \cdot 10^6 \cdot 333} = 4,8 \text{ pF}$$



$$Z_p = \frac{1000 \times (-j333)}{1000 - j333} = \frac{1000 \cdot 333 \angle -90^\circ}{1053,99 \angle -18,42^\circ}$$

$$= 315,94 \cancel{-} 71,57$$

$$= 99,88 - j299,74$$

$$Z_s = 100 + j300$$


$$Z_p = 99,88 - j299,74$$

$$Z_s = Z_p^\dagger$$

Rancang IMC berbentuk L di frekuensi 10 MHz yg meloloskan frekuensi tinggi dengan $R_s = 100\Omega$ dan $R_L = 10\Omega$

Jawab:

$R_s > R_L \rightarrow$ IMC L konan HPF

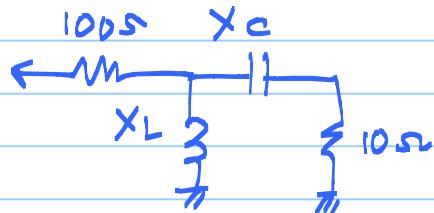

$$Q_s = \frac{X_s}{R_s} \Rightarrow X_s = Q_s \times R_s$$

$$X_s = Q \times R_L = 3 \times 10 = 30$$


$$C = \frac{1}{30 \times 2\pi f} = 530,5 \text{ pF}$$

$$Q = \sqrt{\frac{100}{10}} - 1 = 3$$

$$Q_p = \frac{R_p}{X_p} \rightarrow X_p = \frac{R_p}{Q_p} \Rightarrow X_L = \frac{R_s}{Q} = \frac{100}{3} = 33,3$$

$$L = \frac{33,3}{2\pi f} = \frac{33,3}{2\pi 10 \cdot 10^6} = 530,5 \text{ nH}$$

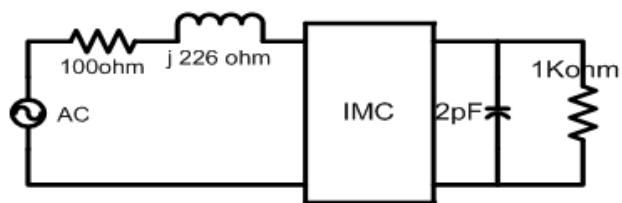Dengan menggunakan metode absorpsi, rancanglah IMC bentuk "L" pada 100MHz dengan sifat meloloskan sinyal DC pada rangkaian berikut:



$$Q_p = Q_s = \sqrt{\frac{R_p}{R_s} - 1} = \sqrt{\frac{1000}{100} - 1} = 3$$


$$Q_s = \frac{X_s}{R_s} \rightarrow X_s = 3 \times 100 = 300$$

$$X_L = X_s - j226 = j300 - j226$$

$$= j74$$

$$2\pi f_r L = j74$$
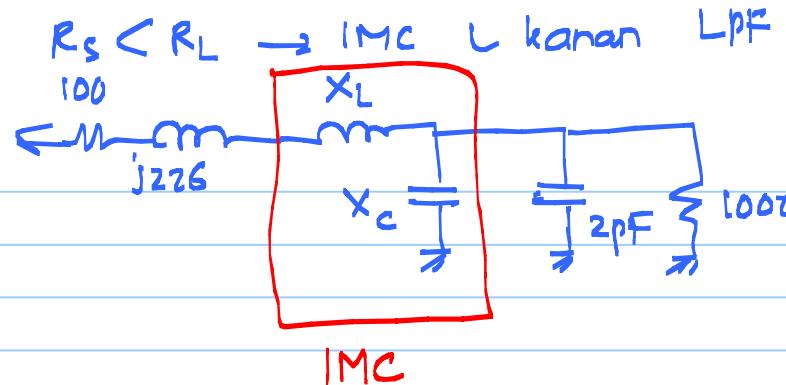
$$L = \frac{j74}{2\pi \cdot 100 \cdot 10^6} = 117 \text{ nH}$$



$$Q_p = \frac{R_p}{X_p} \Rightarrow X_p = \frac{1000}{3} = 333$$

$$\frac{1}{2\pi f_r C} = 333 \rightarrow C = \frac{1}{333 \cdot 2\pi \cdot 100 \cdot 10^6}$$


$$C = 4,8 \text{ pF}$$

$$C_{\pi} = 2 \text{ pF} + C_p$$


$$C_p = 4,8 \text{ pF} - 2 \text{ pF} = 2,8 \text{ pF}$$

Rancang IMC yg meloloskan sinyal DC di $f = 25 \text{ MHz}$ dengan impedansi sumber sebesar $(100 + j100) \Omega$ dan impedansi beban output 1000Ω dan $1,2 \text{ pF}$ paralel.

Jawab :

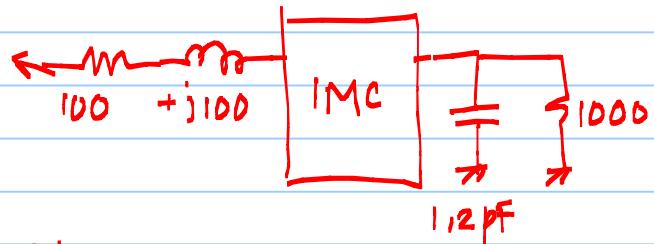

$$R_s < R_L$$

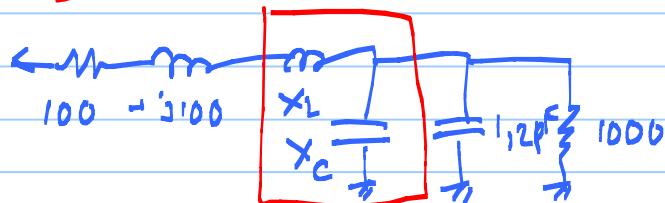

IMC L Kirri
LPF

$$Q = \sqrt{\frac{1000}{100} - 1} = 3$$

$$Q_3 = \frac{X_S}{R_S} \Rightarrow X_S = Q_3 \times R_S = Q \times 100 = 300$$

$$X_{L1} = 300$$

$$X_L = 300 - 100 = 200 \Omega$$


$$L = \frac{200}{2\pi f} = \frac{200}{2\pi \cdot 25 \cdot 10^6} = 1,27 \text{ nH}$$

$$Q_p = \frac{R_p}{X_p} \Rightarrow X_p = \frac{R_p}{Q} = \frac{1000}{3} = 333,3$$

$$C_t = \frac{1}{333,3 \times 2\pi f} = 19,1 \text{ pF}$$

$$C = 19,1 \text{ pF} - 1,2 \text{ pF} = 17,9 \text{ pF}$$

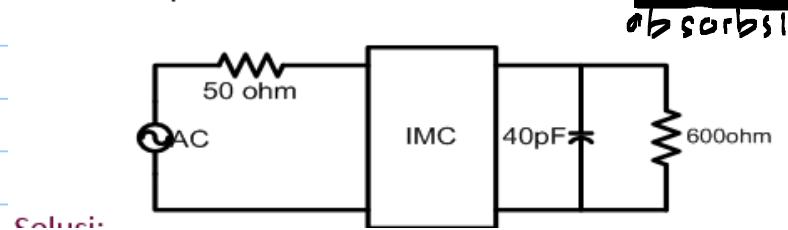Rancanglah suatu IMC yang dapat memblock sinyal DC antara beban-sumber rangkaian dibawah ini, pada frekuensi operasi 75 MHz. Gunakan metode [REDACTED]



cari...


$$Q_p = \frac{R_p}{X_p} \Rightarrow X_p = \frac{R_p}{Q_p} = \frac{600}{7,32} = 180,7$$

$$\frac{jX_L}{\frac{1}{j\omega C}} = -j53 \Rightarrow j180,7 = \frac{jX_L \times (-j53)}{jX_L - j53} = \frac{53X_L}{j(X_L - 53)}$$

$$-180,7(X_L - 53) = 53X_L$$

$$-180,7X_L + 9577,1 = 53X_L$$
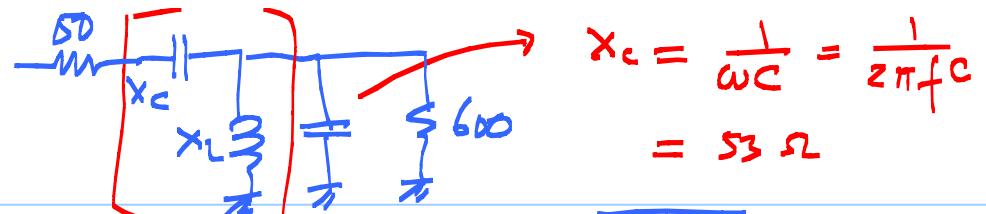
$$X_L = \frac{9577,1}{53 + 180,7} = 40,98 \Rightarrow L = \frac{40,98}{2\pi f} = 66,9 \text{ nH}$$



IMC L Kiri

HPF

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} \\ = 53 \text{ } \Omega$$


$$Q = \sqrt{\frac{600}{50}} - 1 = 3,32$$

$$Q_S = \frac{X_S}{R_S} \Rightarrow X_S = Q_S \cdot R_S$$

$$X_C = Q \cdot 50 = 166$$

$$C = \frac{1}{2\pi f 166} = 12,78 \text{ PF}$$

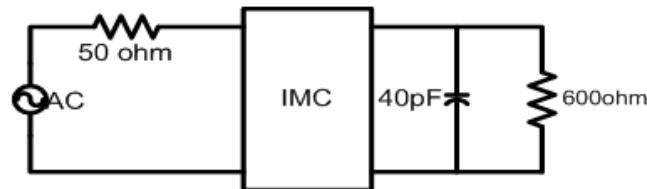Rancanglah suatu IMC yang dapat memblock sinyal DC antara beban-sumber rangkaian dibawah ini, pada frekuensi operasi 75 MHz. Gunakan metode resonansi.



Solusi:

$$Q_p = Q_s = \sqrt{\frac{R_s}{R_p}} - 1 = \sqrt{\frac{600}{50}} - 1 = 3,32$$


$$Q_s = \frac{X_s}{R_s} \rightarrow X_s = 50 \times 3,32 = 165,83$$

$$\frac{1}{2\pi f_c C} = 165,83 \rightarrow C = \frac{1}{2\pi \cdot 75 \cdot 10^6 \cdot 165,83} = 12,8 \text{ pF}$$


$$Q_p = \frac{R_p}{X_p} \rightarrow X_p = \frac{600}{3,32} = 180,72$$

$$L = \frac{180,72}{2\pi \cdot 75 \cdot 10^6} = 383,5 \text{ nH}$$
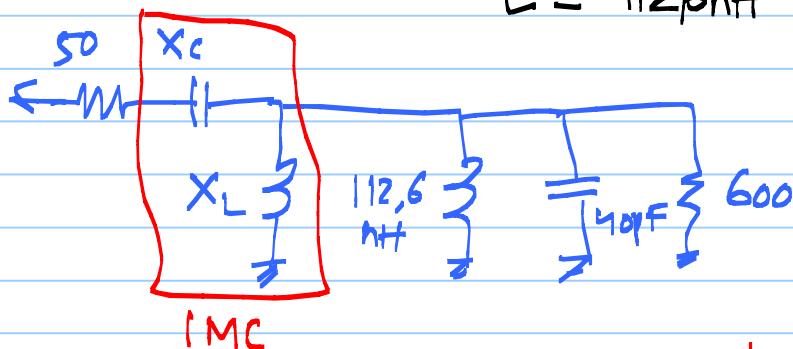
$$f_r = \frac{1}{2\pi\sqrt{LC}} \rightarrow L = \frac{1}{\omega_r^2 C} = \frac{1}{(2\pi \cdot 75 \cdot 10^6)^2 \cdot 40 \cdot 10^{-12}} \\ L = 112,6 \text{ nH}$$



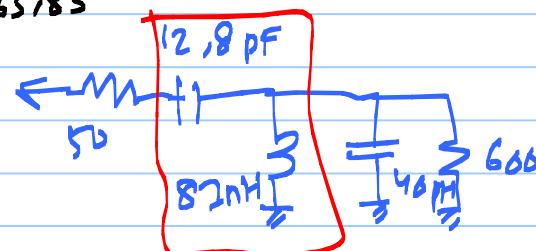
$$L_t = \frac{L_1 \times L_2}{L_1 + L_2} \\ = \frac{112,6 \text{ nH} \cdot 383,5 \text{ nH}}{112,6 \text{ nH} + 383,5 \text{ nH}}$$



$$= 87 \text{ nH}$$

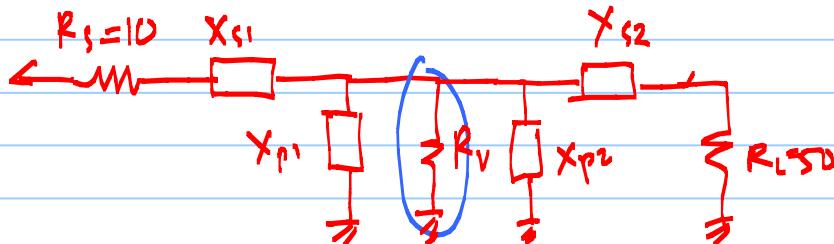- Rancanglah 4 kemungkinan konfigurasi IMC bentuk "T" untuk menyepadankan $R_s=10\Omega$ dan $R_L=50\Omega$ dengan $Q=10$.



$$Q = \sqrt{\frac{R_V}{R_{kecil}}} - 1$$

$$R_V = R_{kecil} (1+Q^2) = 10 (1+10^2) = 1010 \Omega$$


$$Q_s = \frac{X_{s1}}{R_s} \Rightarrow X_{s1} = Q_s \times R_s = 10 \times 10 = 100 \Omega$$

$$Q_p = \frac{R_p}{X_{p1}} \Rightarrow X_{p1} = \frac{R_p}{Q_p} = \frac{1010}{10} = 101 \Omega$$


$$Q = \sqrt{\frac{R_V}{R_L}} - 1 = \sqrt{\frac{1010}{50}} - 1 = 4,38$$

$$Q_p = \frac{R_p}{X_{p2}} \rightarrow X_{p2} = \frac{R_p}{Q_p} = \frac{1010}{4,38} = 231 \Omega$$
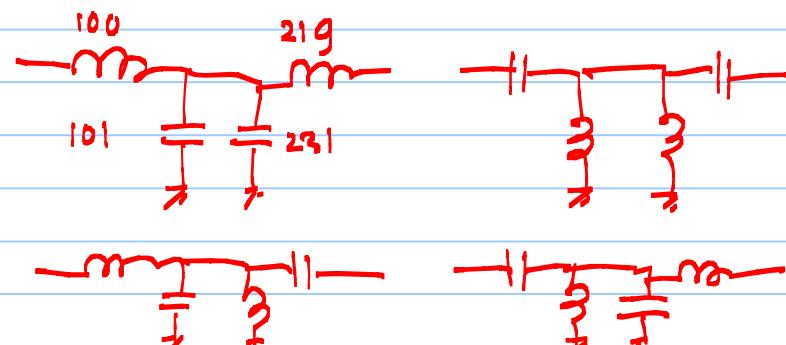
$$Q_s = \frac{X_{s2}}{R_L} \rightarrow X_{s2} = Q_s \times R_{s2} = 4,38 \times 50 = 219 \Omega$$



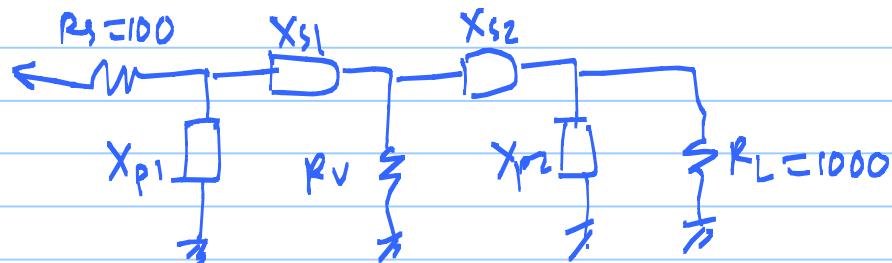- Rancanglah 4 kemungkinan konfigurasi IMC bentuk "Π" yang menyepadankan $R_s = 100\Omega$, $R_L = 1000\Omega$, dengan faktor kualitas $Q = 15$.



$$Q = \sqrt{\frac{R_{buar}}{R_v} - 1} \Rightarrow R_v = \frac{R_{buar}}{1+Q^2} = \frac{100}{1+15^2}$$

$$R_v = 4,42$$

$$Q = \sqrt{\frac{R_s}{R_v} - 1} = \sqrt{\frac{100}{4,42} - 1} = 4,65$$

$$Q_s = \frac{X_s1}{R_v} \Rightarrow X_s1 = Q_s \times R_v = 4,65 \times 4,42 = 20,55 \Omega$$

$$Q_p = \frac{R_p}{X_p1} \Rightarrow X_p1 = \frac{R_p}{Q_p} = \frac{100}{4,65} = 21,5 \Omega$$

$$Q_p = \frac{R_p}{X_p2} \Rightarrow X_p2 = \frac{R_p}{Q_p} = \frac{100}{15} = 6,67 \Omega$$

$$Q_s = \frac{X_s2}{R_v} \Rightarrow X_s2 = Q_s \times R_v = 15 \times 4,42 = 66,3 \Omega$$

