
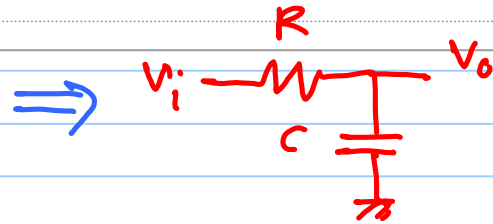


Desain Filter Aktif

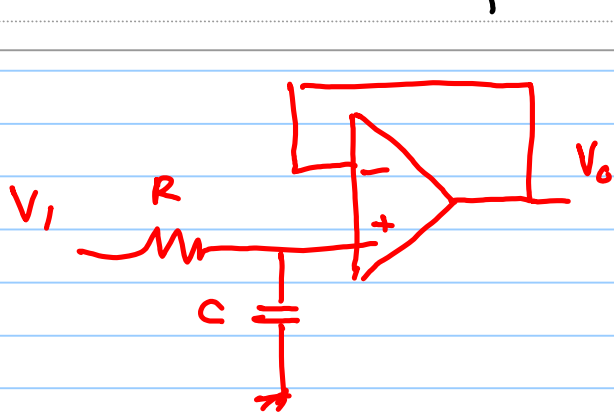


$$\frac{V_o}{V_i} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{1}{1 + sCR} = \frac{1}{1 + \frac{s}{1/CR}}$$

$$\omega_0 = \frac{1}{CR} \quad \text{atau}$$

$$\frac{V_o}{V_i} = \frac{1}{1 + sCR} = \frac{1/RC}{s + 1/RC}$$

$$\omega_0 = \frac{1}{RC} \Rightarrow \frac{V_o}{V_i} = \frac{\omega_0}{s + \omega_0}$$
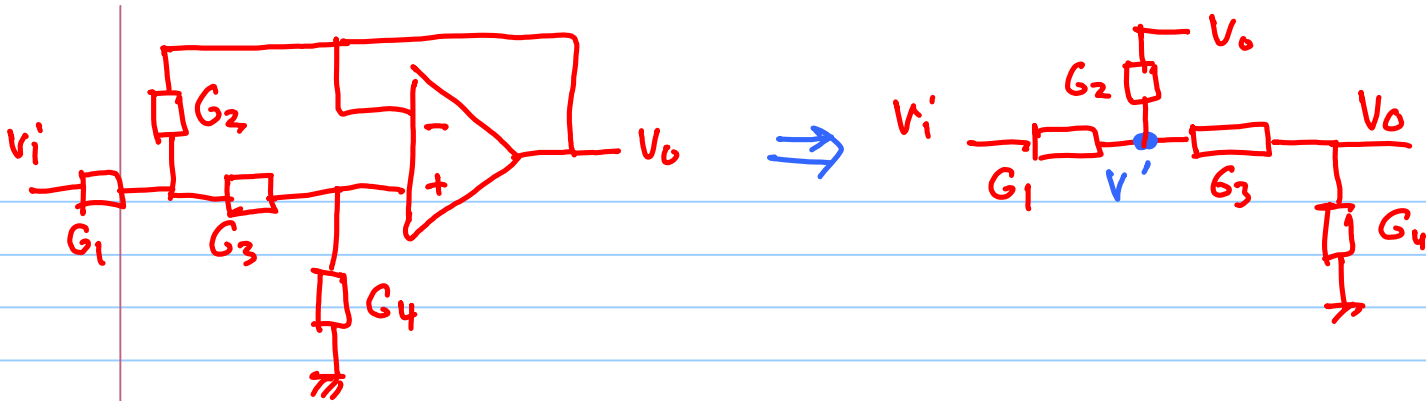
$$\text{Normalisasi: } \omega_0 = 1 \Rightarrow \frac{V_o}{V_i} = \frac{1}{s+1} \leftarrow \text{orde 1}$$



$$V_0 = \frac{\frac{1}{G_4}}{\frac{1}{G_4} + \frac{1}{G_3}} \cdot V'$$

$$V_0 = \frac{G_3}{G_3 + G_4} V'$$

$$V' = \frac{G_3 + G_4}{G_3} V_0 \dots (1)$$

Node \$V'\$:

$$(V' - v_i) G_1 + (V' - V_0) G_3 + (V' - V_0) G_2 = 0$$

$$V' (G_1 + G_2 + G_3) = v_i G_1 + V_0 (G_2 + G_3) \dots (2)$$

Substituting (1) & (2):


$$V_0 \frac{G_3 + G_4}{G_3} (G_1 + G_2 + G_3) = v_i G_1 + V_0 (G_2 + G_3)$$

$$V_0 (G_3 + G_4) (G_1 + G_2 + G_3) = v_i G_1 G_3 + V_0 G_3 (G_2 + G_3)$$

$$V_o \left[(G_3 G_1 + G_3 G_2 + G_3^2 + G_4 G_1 + G_4 G_2 + G_4 G_3) - (G_5 G_2 + G_5^2) \right] = V_i G_1 G_3$$

$$\frac{V_o}{V_i} = \frac{G_1 G_3}{G_4 G_1 + G_4 G_2 + G_4 G_3 + G_1 G_3}$$

Contoh : LPF

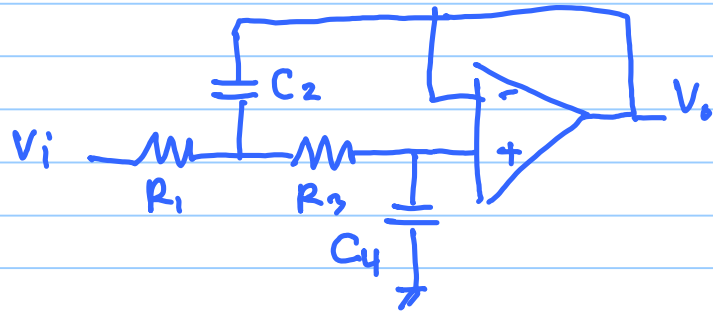

$$\begin{aligned} \frac{V_o}{V_i} &= \frac{G_1 G_3}{G_4 G_1 + G_4 G_2 + G_4 G_3 + G_1 G_3} \\ &= \frac{\frac{1}{R_1} \cdot \frac{1}{R_3}}{sC_4 \frac{1}{R_1} + sC_4 sC_2 + sC_4 \frac{1}{R_3} + \frac{1}{R_1} \cdot \frac{1}{R_3}} \\ &= \frac{1/R_1 R_3}{s^2 C_2 C_4 + sC_4 \left(\frac{1}{R_1} + \frac{1}{R_3} \right) + 1/R_1 R_3} \end{aligned}$$

$$\frac{V_o}{V_i} = \frac{\frac{1}{R_1 R_3 C_2 C_4}}{s^2 + s \frac{1}{C_2} \left(\frac{1}{R_1} + \frac{1}{R_3} \right) + \frac{1}{R_1 R_3 C_2 C_4}}$$

Normalisasi $\omega_0^2 = 1 = \frac{1}{C_2 C_4}$

$$\frac{V_o}{V_i} = \frac{1}{s^2 + s \frac{2}{C_2} + 1} \quad \leftarrow \text{orde 2}$$

Penarrangan lainnya:

Normalisasi R dalam 1Ω dan C dalam 1F

$$R_1 R_3 C_2 C_4 = 1$$

Nilai $R_1 = R_3 = 1\Omega$, maka $C_2 C_4 = 1$

$$\frac{1}{C_2} \left(\frac{1}{R_1} + \frac{1}{R_3} \right) = 1,414$$

$$\Rightarrow \frac{2}{C_2} = 1,414 \Rightarrow C_2 = 1,414 \text{ F}$$

$$C_4 = \frac{1}{C_2} = 0,707 \text{ F}$$

Normalisasi thd $R_1 = R_3 = 1\Omega$

$$\frac{V_o}{V_i} = \frac{\frac{1}{C_2 C_4}}{s^2 + s \frac{2}{C_2} + \frac{1}{C_2 C_4}}$$

Butterworth Pole Locations

Order	Real -a	Imaginary +/-jb
2	0.7071	0.7071
3	0.5000 1.0000	0.8660

Normalized Butterworth


- The order of the filter is given by the normalized denominator of the transfer function known as normalized Butterworth polynomial.

Order of Filter	Butterworth Polynomial
1	$(s+1)$
2	$s^2 + 1.414s + 1$
3	$(s+1)(s^2 + s + 1)$
4	$(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)$
5	$(s+1)(s^2 + 0.618s + 1)(s^2 + 1.618s + 1)$

Bila $R_1 = R_3 = 1k\Omega$, maka $C_2 = \frac{C_{2n}}{2\pi f \times R_1} = \frac{1,418}{2\pi \cdot 1000 \cdot 1000} = 226 \text{ nF}$

frekuensi cut off ←
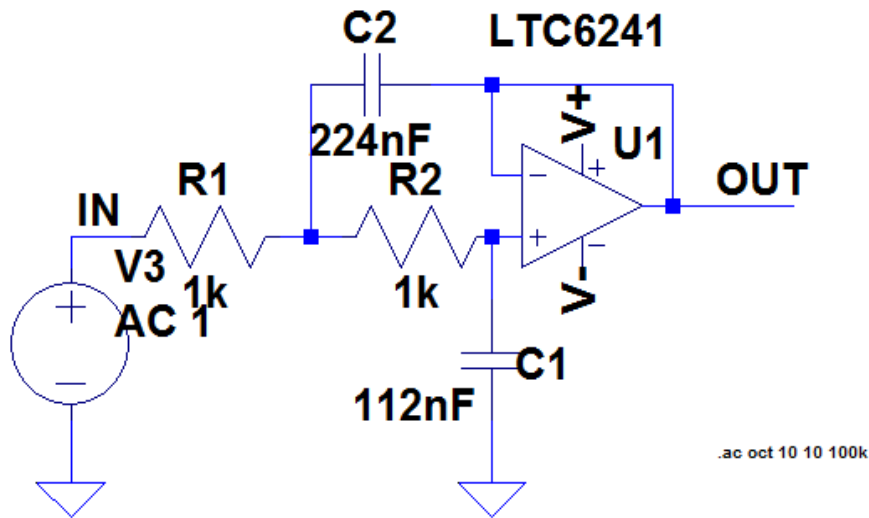
$$C_4 = \frac{C_{4n}}{2\pi f \times R} = \frac{0,705}{2\pi \cdot 1000 \cdot 1000} = 114 \text{ nF}$$




n (order)	Normalized Denominator Polynomials in Factored Form
1	(1+s)
2	(1+1.414s+s ²)
3	(1+s)(1+s+s ²)
4	(1+0.765s+s ²)(1+1.848s+s ²)
5	(1+s)(1+0.618s+s ²)(1+1.618s+s ²)
6	(1+0.518s+s ²)(1+1.414s+s ²)(1+1.932s+s ²)
7	(1+s)(1+0.445s+s ²)(1+1.247s+s ²)(1+1.802s+s ²)
8	(1+0.390s+s ²)(1+1.111s+s ²)(1+1.663s+s ²)(1+1.962s+s ²)
9	(1+s)(1+0.347s+s ²)(1+s+s ²)(1+1.532s+s ²)(1+1.879s+s ²)
10	(1+0.313s+s ²)(1+0.908s+s ²)(1+1.414s+s ²)(1+1.782s+s ²)(1+1.975s+s ²)

Filter orde 3 LPF

$$(s+1)(s^2+s+1)$$


\downarrow \downarrow
 orde 1 orde 2

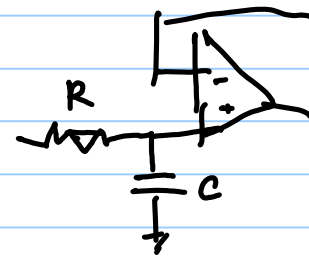

$$\Rightarrow \omega_0 = \frac{1}{RC} \Rightarrow \omega_0 = 1$$

$$RC = 1$$

$$R = 1\Omega \Rightarrow C = 1F$$

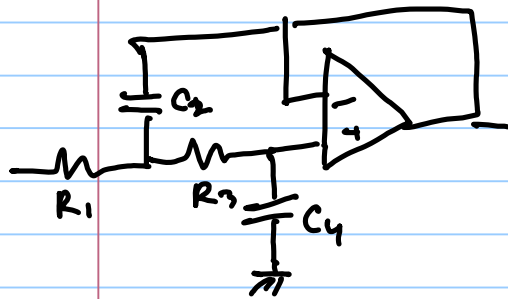

$$\omega_0^2 = \frac{1}{R_1 R_3 C_2 C_4} = 0$$

$$R_1 R_3 C_2 C_4 = 1$$

$$R_1 = R_3 = 1\Omega$$

$$C_2 C_4 = 1$$

$$\frac{1}{C_2} \left(\frac{1}{R_1} + \frac{1}{R_3} \right) = 1$$

$$C_2 = 2F$$

$$C_4 = 0,5F$$

sehingga :


Jika $R_1 = R_3 = 1k$

$$C = \frac{C_n}{2\pi f \cdot R} = \frac{1}{2\pi \cdot 1000 \cdot 1000} = 159,2 \text{ nF}$$

$$C_2 = \frac{C_{in}}{2\pi f R} = \frac{2}{2\pi \cdot 1000 \cdot 1000} = 318,3 \text{ nF}$$

$$C_4 = \frac{C_{in}}{2\pi f R} = \frac{0,5}{2\pi \cdot 1000 \cdot 1000} = 79,6 \text{ nF}$$

High Pass Filter (HPF)

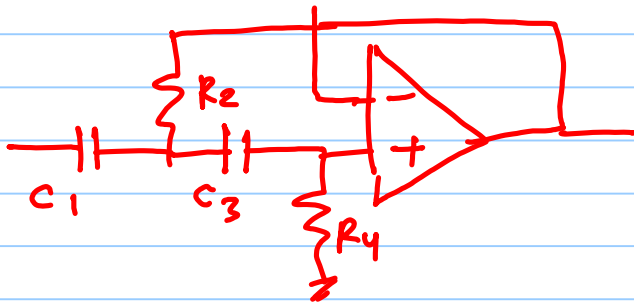

Normalisasi thd $C_1 = C_3 = 1F$

$$\frac{V_o}{V_i} = \frac{G_1 G_3}{G_4 G_1 + G_4 G_2 + G_4 G_3 + G_1 G_3}$$

$$\frac{V_o}{V_i} = \frac{s C_1 s C_3}{\frac{1}{R_4} \cdot s C_1 + \frac{1}{R_4} \cdot \frac{1}{R_2} + \frac{1}{R_4} \cdot s C_3 + s C_1 s C_3}$$

$$\frac{V_o}{V_i} = \frac{s^2 C_1 C_3}{s^2 C_1 C_3 + s \cdot \frac{1}{R_4} (C_1 + C_3) + \frac{1}{R_4} \cdot \frac{1}{R_2}}$$

$$\frac{V_o}{V_i} = \frac{s^2}{s^2 + s \frac{2}{R_4} + \frac{1}{R_4} \cdot \frac{1}{R_2}}$$

Butterworth Pole Locations

Order	Real -a	Imaginary +/-jb
2	0.7071	0.7071
3	0.5000 1.0000	0.8660

$$\frac{V_o}{V_i} = \frac{s^2 R_2 R_4}{s^2 R_2 R_4 + s^2 R_2 + 1}$$

$$-0.7071 \pm j0.7071 = -(0.7071 \pm j0.7071) \cdot \frac{(-0.7071 \pm j0.7071)}{(-0.7071 \pm j0.7071)}$$

$$= \frac{0.999}{-0.7071 \pm j0.7071}$$

$$\text{Invert} \Rightarrow \frac{-0.7071 \pm j0.7071}{0.999} = -0.7071 \pm j0.7071$$

Poles

$$-0.7071 \pm j0.7071 \Rightarrow s^2 + 1.414s + 1 \Rightarrow s^2 + 1.414s + 1$$

$$2R_2 = 1.414$$

$$R_2 = 0.707$$

$$R_4 = \frac{1}{R_2} = \frac{1}{0.707} = 1.414$$

$$C_1 = C_3 = 1F$$

$$R_2 = 0,7007$$

$$R_4 = 1,4014$$

Jika $C_1 = C_3 = 1nF$, maka $R_2 = \frac{R_{un}}{2\pi f C} = \frac{0,7007}{2\pi \cdot 1000 \cdot 10^{-9}} = 111,5 k\Omega$

$$R_4 = \frac{R_{un}}{2\pi f C} = \frac{1,4014}{2\pi \cdot 1000 \cdot 10^{-9}} = 223 k\Omega$$

Perancangan HPF Butterworth orde 3

Butterworth Pole Locations

Order	Real -a	Imaginary +/-jb
2	0.7071	0.7071
3	0.5000 1.0000	0.8660

Pole : $-0,500 \pm j0,866 \rightarrow$ double pole

$-1,000 \rightarrow$ single pole

$$\frac{V_o}{V_i} = \frac{s^2 R_2 R_4}{s^2 R_2 R_4 + s^2 R_2 + 1}$$

$$-0,500 \pm j0,866 \Rightarrow -(0,500 \pm j0,866) \times \frac{(0,500 + j0,866)}{(0,500 \pm j0,866)}$$

$$= \frac{0,9999}{0,500 \pm j0,866} =$$

$$\text{Invertirung} \Rightarrow -0,5 \pm j0,866$$

Double pole : $-0,5 \pm j0,866$

$$(s + 0,5 + j0,866)(s + 0,5 - j0,866)$$

$$s^2 + s + 1$$

Normalisasi: $C_1 = C_3 = 1\text{F}$, maka : $2R_2 = 1 \Rightarrow R_2 = 0,5 \Omega \Rightarrow R_2 R_4 = 1 \Rightarrow R_4 = 2 \Omega$


Selanjutnya jika $f = 1\text{kHz}$ dgn nilai $C_1 = C_3 = 1\text{nF}$

$$\text{maka : } R_2 = \frac{R_{un}}{2\pi f C} = \frac{0,5}{2\pi \cdot 1000 \cdot 10^{-9}} = 79,5 \text{ k}\Omega$$


$$R_4 = \frac{R_{un}}{2\pi f} = \frac{2}{2\pi \cdot 1000 \cdot 10^{-9}} = 318 \text{ k}\Omega$$

Single pole : $-1,000$

MoKa :

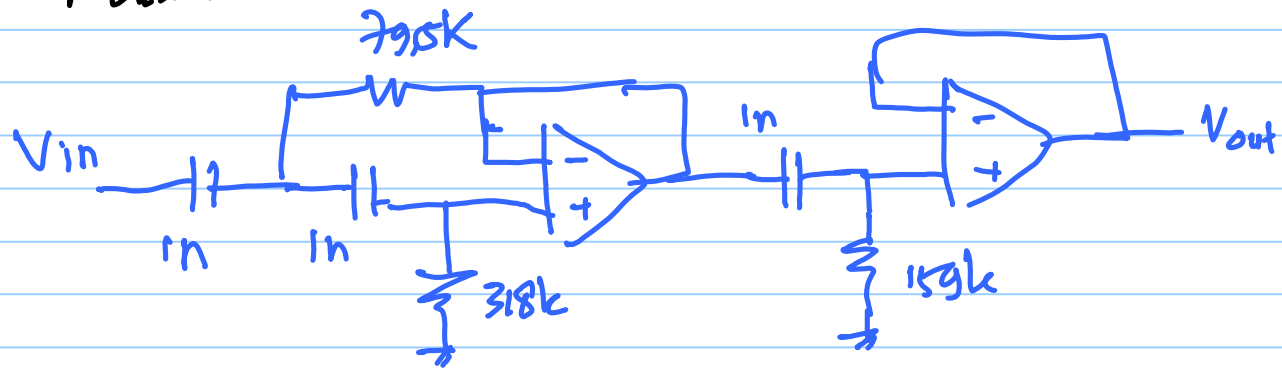

Band Pass Filter

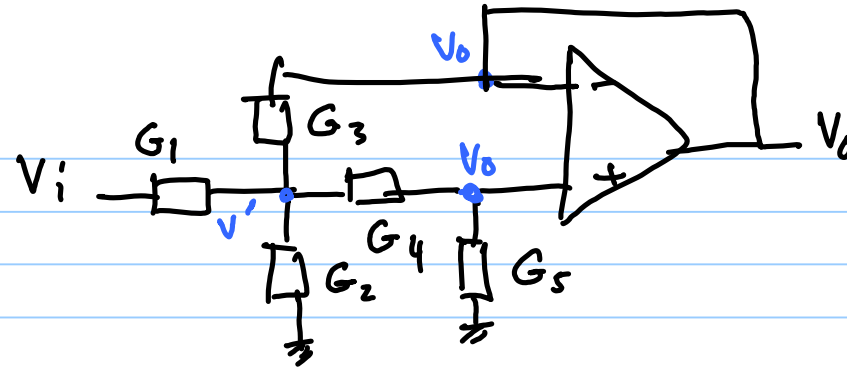

$$V_o = \frac{G_4}{G_4 + G_5} \cdot V'$$

$$V' = \frac{G_4 + G_5}{G_4} \cdot V_o$$

Node voltage V' :

$$(V' - V_i) G_1 + (V' - V_o) G_3 + (V' - 0) G_2 + (V' - V_o) G_4 = 0$$


$$V' (G_1 + G_2 + G_3 + G_4) - V_o (G_3 + G_4) = V_i G_1$$

$$(G_4 + G_5) V_o (G_1 + G_2 + G_3 + G_4) - V_o (G_3 + G_4) = V_i G_1$$

$$V_o \left(\overset{G_4}{G_4 G_1 + G_4 G_2 + \cancel{G_4 G_3} + \cancel{G_4^2}} + G_5 G_1 + G_5 G_2 + G_5 G_3 + G_5 G_4 - \cancel{G_3 G_4} - \cancel{G_4^2} \right) = V_i G_1 G_4$$

$$\frac{V_o}{V_i} = \frac{G_1 G_4}{G_5 (G_1 + G_2 + G_3 + G_4) + G_4 (G_1 + G_2)}$$
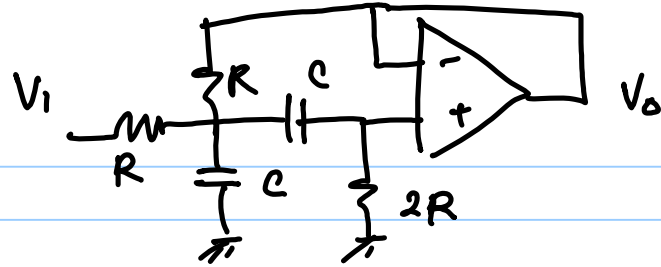
$$\frac{V_o}{V_i} = \frac{G_1 G_4}{G_3 (G_1 + G_2 + G_3 + G_4) + G_4 (G_1 + G_2)}$$



$$\frac{V_o}{V_i} = \frac{\frac{1}{R} sC}{\frac{1}{2R} \left(\frac{1}{R} + sC + \frac{1}{R} + sC \right) + sC \left(\frac{1}{R} + sC \right)} = \frac{\frac{sC}{R}}{\frac{1}{2R} \left(\frac{2}{R} + 2sC \right) + sC \left(\frac{1}{R} + sC \right)} = \frac{\frac{sC}{R}}{\frac{1}{R^2} + \frac{sC}{R} + \frac{sC}{R} + s^2 C^2}$$

$$\frac{V_o}{V_i} = \frac{\frac{sC}{R}}{s^2 C^2 + 2 \frac{sC}{R} + \frac{1}{R^2}} = \frac{\cancel{C^2} \frac{s}{RC}}{\cancel{C^2} \left(s^2 + \frac{2s}{RC} + \frac{1}{C^2 R^2} \right)} = \frac{s \cdot \frac{1}{RC}}{s^2 + 2s \cdot \frac{1}{RC} + \left(\frac{1}{RC} \right)^2}$$

desidero $\omega_0 = \frac{1}{RC} \Rightarrow \frac{V_o}{V_i} = \frac{\omega_0 s}{s^2 + 2s\omega_0 + \omega_0^2} \leftarrow \text{ord } 2$

BPF orde 2 Butterworth

$$\frac{V_o}{V_i} = \frac{s \cdot \frac{1}{RC}}{s^2 + 2s \cdot \frac{1}{RC} + \left(\frac{1}{RC}\right)^2} \leftarrow s^2 + 1,414s + 1 \Rightarrow \frac{2}{RC} = 1,414$$

Jika $R = 1\Omega$, maka $C = \frac{2}{1,414} = 1,414F$

sehingga jika $R = 1k\Omega$ maka

$$C = \frac{1,414}{2 \cdot 1000 \cdot 1000} = 225nF$$

